

SNAP JOURNAL

NAME _____

SNAP CIRCUIT TITLE OR NUMBER _____

Sketch Your Circuit. Refer to page 43 for Schematic Symbols in the Student Guide.

	1	2	3	4	5	6	7	8	9	10
A										
B										
C										
D										
E										
F										
G										

What did you learn about circuits from doing this activity? _____
